

# Digital Logic Design + Computer Architecture

Sayandeep Saha

Assistant Professor  
Department of Computer  
Science and Engineering  
Indian Institute of Technology  
Bombay






# Sequential Circuits



# A Circuit that Remembers


- How do you remember things?
  - Memory
- Can we design a circuit which remembers?
  - A formal way to model this capability is called a **state**
  - So we will be modelling circuits to create a **state**.

**Remember**

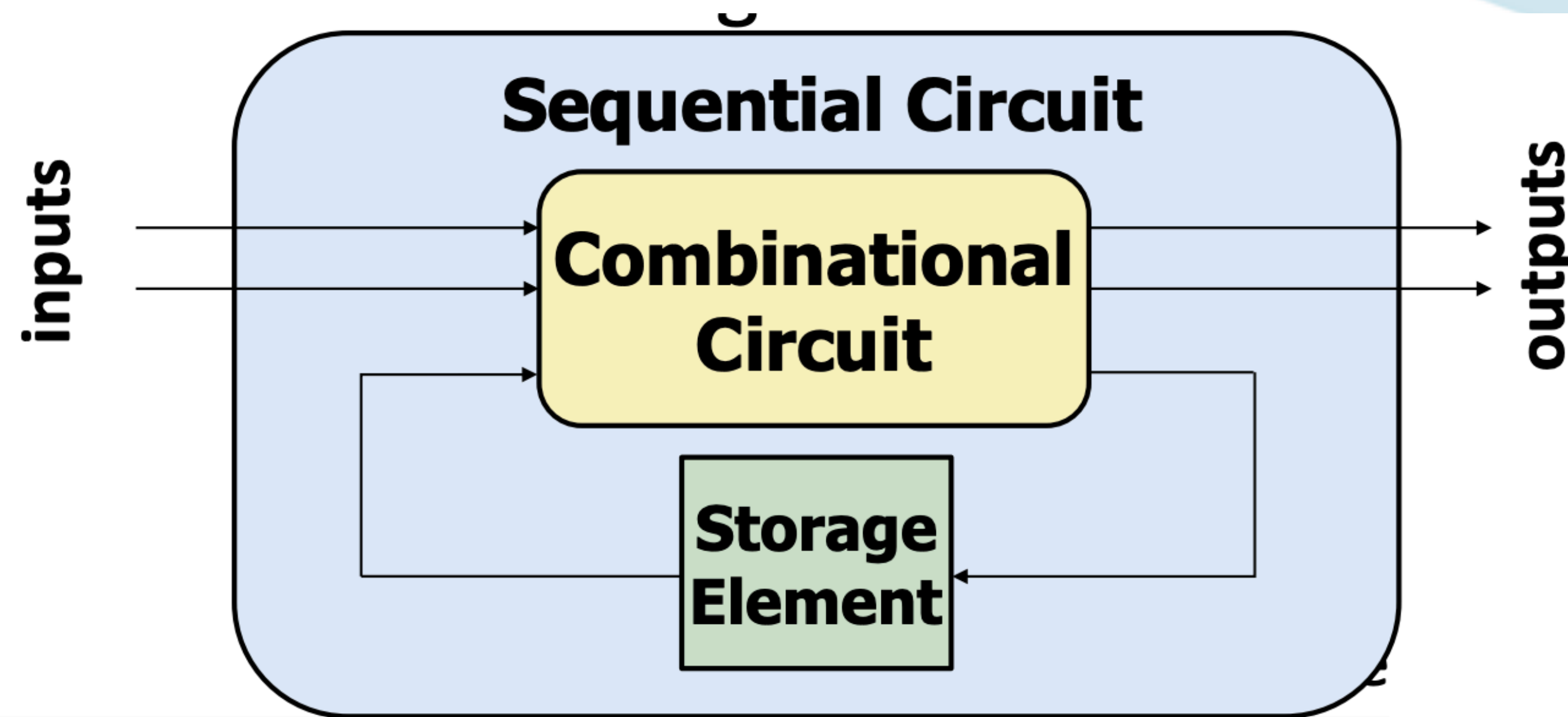

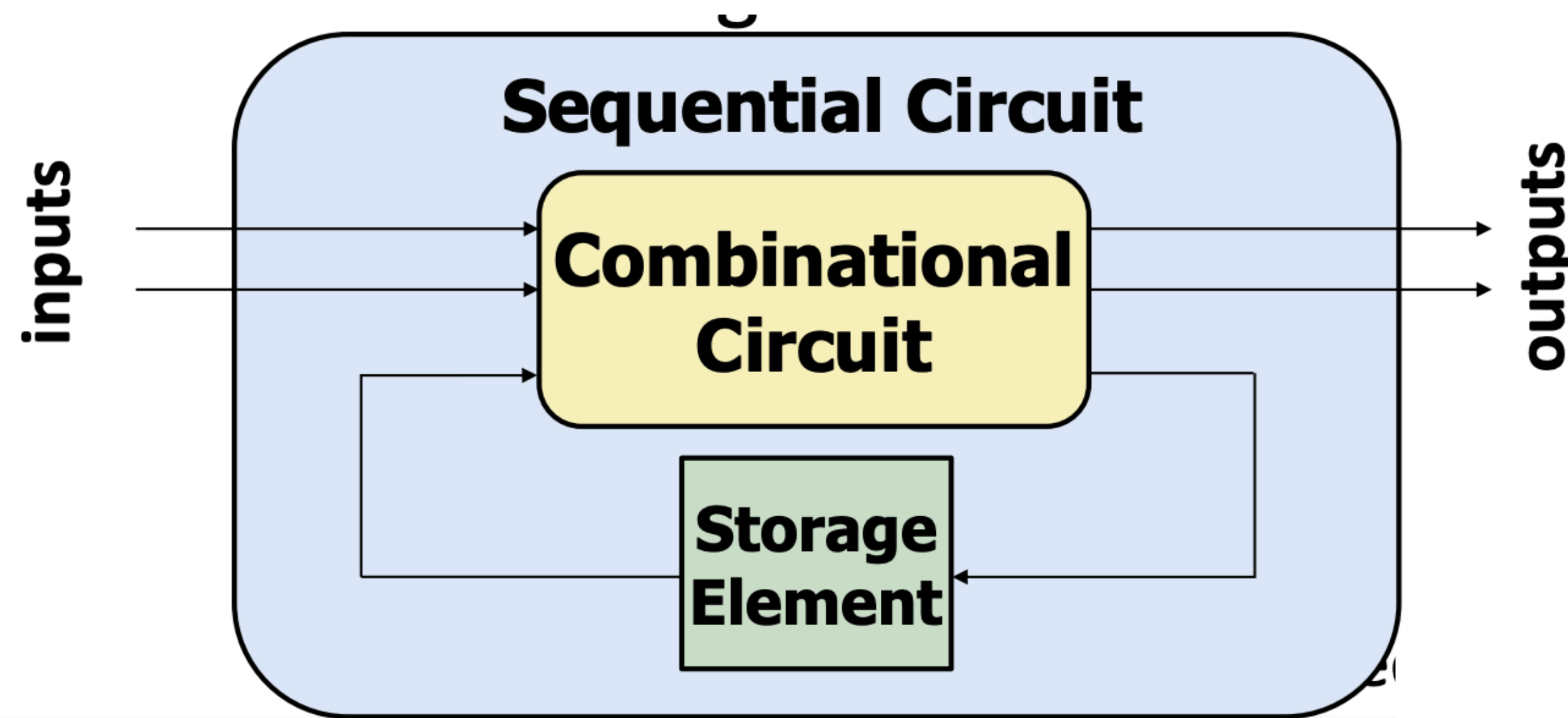
# A Circuit that Remembers

- **Every digital logic you see in real life is sequential**
  - Your processors — that you going to see in the rest of the course
  - Your washing machine — it remembers your setting and washes accordingly
  - Your elevator — it remembers which floors to stop
  - Your ATM machine — it remembers your choice and updates your account after despatching money



# Sequential Circuits

 


# Sequential Circuits

To generate the  $Y$ 's: memory devices must be supplied with appropriate input values

- **Characteristic table/functions:** switching functions that describe the impact of  $x_i$ 's and  $y_j$ 's on the memory-element input
- **Excitation table:** its entries are the values of the memory-element inputs

Most widely used memory elements: **flip-flops**, which are made of **latches**

 - **Latch:** remains in one state indefinitely until an input signals directs it to do otherwise




# Memory Element: Latches

**Latch:** remains in one state indefinitely until an input signals directs it to do otherwise


**Set-reset of *SR* latch:**



(a) Block diagram.

 

(b) NOR latch.

 

(c) NAND latch.

# Memory Element: Latches

Characteristic table and excitation requirements:

$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1


$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$


<i>Circuit change</i>		<i>Required value</i>	
<i>From:</i>	<i>To:</i>	$S$	$R$
0	0	0	—
0	1	1	0
1	0	0	1
1	1	—	0

**Clocked  $SR$  latch:** all state changes synchronized to clock pulses

 - Restrictions placed on the length and frequency of clock pulses: so that the circuit changes state no more than once for each clock pulse



(a) Block diagram.

 

(b) Logic diagram.



# Memory Element: Latches

Why is the (1,1) input forbidden?

$y(t)$	$S(t)$	$R(t)$	$y(t + 1)$
0	0	0	0
0	0	1	0
0	1	1	?
0	1	0	1
1	1	0	1
1	1	1	?
1	0	1	0
1	0	0	1


$$RS = 0$$

$$y(t + 1) = R'y(t) + S$$

1. If  $R=S=1$ ,  $Q$  and  $Q'$  will both settle to 1, which **breaks** our invariant that  $Q = !Q'$
2. If  $S$  and  $R$  transition back to 0 at the same time,  $Q$  and  $Q'$  begin to oscillate between 1 and 0 because their final values depend on each other (**metastability**)
  - This eventually settles depending on **variation in the circuits**



# Memory Element: Latches

 


- A **clock** is a periodic signal that is used to keep time in sequential circuits.
- **Duty Cycle** is the ration of  $t_w/T_{\text{period}}$
- We want to keep  $t_w$  small so that in the same clock pulse only a single computation is performed.
- We want to keep  $T_{\text{period}}$  sufficient so that there is enough time for the next input to be computed.


 
# Memory Element: T Latch

Value 1 applied to its input triggers the latch to change state



(a) Block diagram.

(b) Deriving the T latch from the clocked SR latch.

Excitations requirements:

Circuit change		Required value <i>T</i>
From:	To:	
0	0	0
0	1	1
1	0	1
1	1	0

“Q” is basically “y”

Characteristic Table

T Flip-Flop		
T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement

$$y(t+1) = Ty'(t) + T'y(t) \\ = T\oplus y(t)$$




# Memory Element: JK Latch

Unlike the *SR* latch,  $J = K = 1$  is permitted: when it occurs, the latch acts like a trigger and switches to the complement state



(a) Block diagram.

 

(b) Constructing the JK latch from the clocked SR latch.

## Excitation requirements:

Circuit change		Required value	
From:	To:	<i>J</i>	<i>K</i>
0	0	0	–
0	1	1	–
1	0	–	1
1	1	–	0

“Q” is basically “y”

Can you write the characteristic equation?

## Characteristic Table

<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	<i>Q</i> ( <i>t</i> + 1)	
0	0	<i>Q</i> ( <i>t</i> )	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q</i> '( <i>t</i> )	Complement


$$y(t + 1) = Jy(t)' + K'y(t)$$




# D Latch — The Latch of Your Life

The next state of the  $D$  latch is equal to its present excitation:  
 $y(t+1) = D(t)$

<b><i>D</i> Flip-Flop</b>		
<b><i>D</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	Reset
1	1	Set

 

(a) Block diagram.

 

(b) Transforming the JK latch to the D latch.

Excitation Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1



# How is Your Clock?

**Clocked latch:** changes state only in synchronization with the clock pulse and no more than once during each occurrence of the clock pulse

**Duration of clock pulse:** determined by circuit delays and signal propagation time through the latches


- Must be long enough to allow latch to change state, and
- Short enough so that the latch will not change state twice due to the same excitation

**Excitation of a *JK* latch within a sequential circuit:**

- Length of the clock pulse must allow the latch to generate the  $y$ 's
- But should not be present when the values of the  $y$ 's have propagated through the combinational circuit


**How fast/slow should be the clock really?**

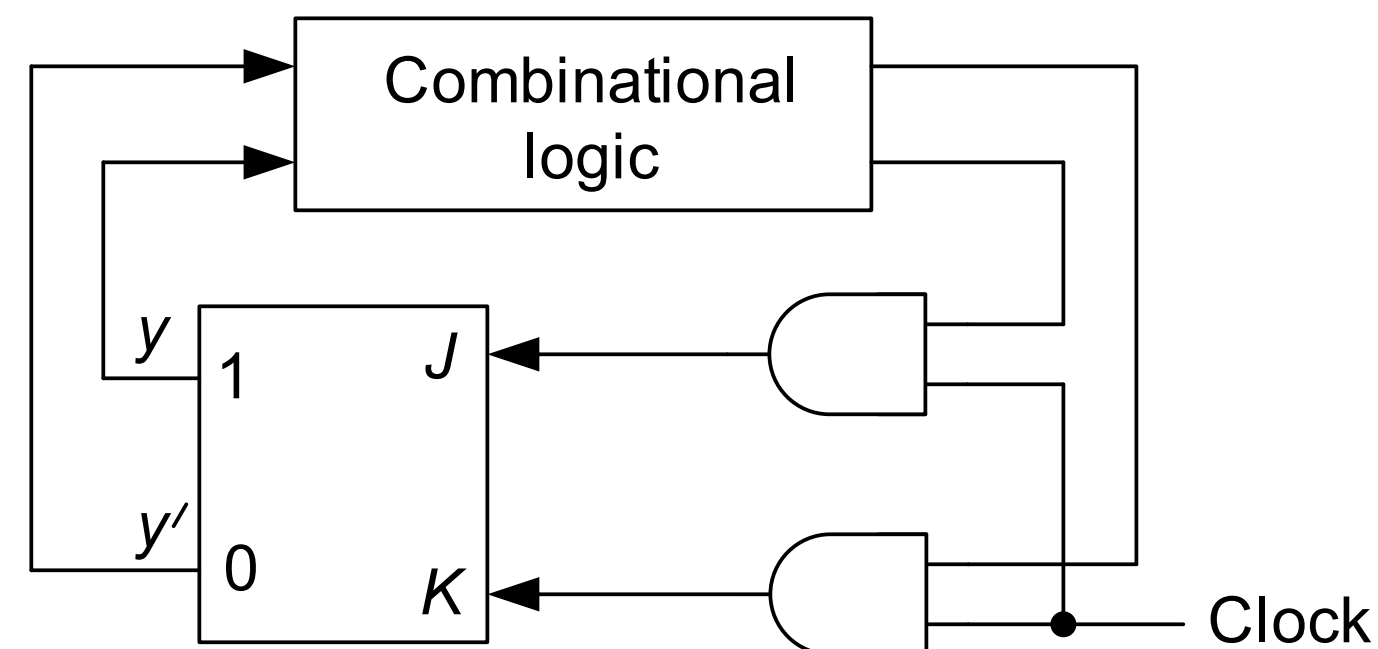**But when does the flip-flop changes its state???**






# All in One

 

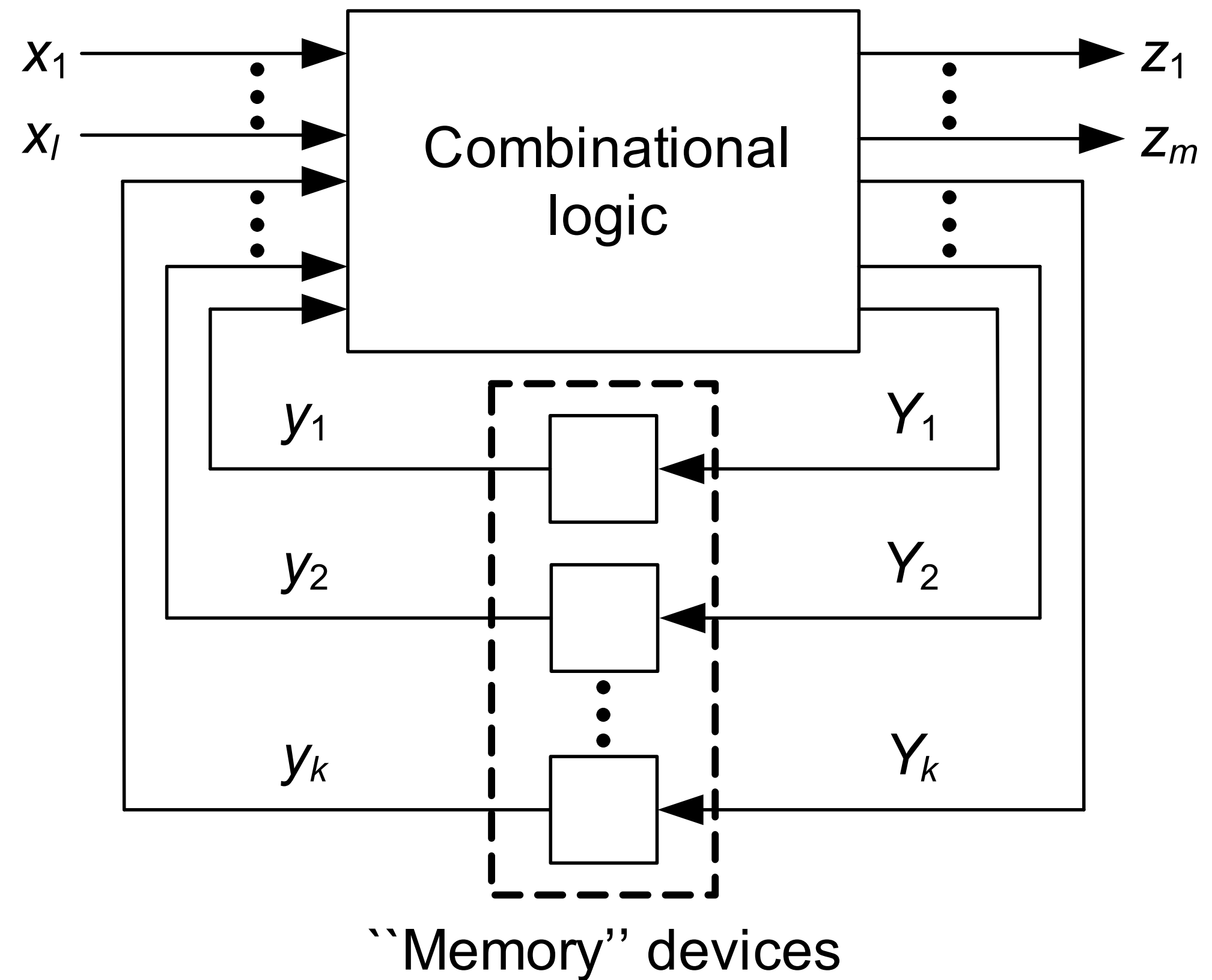**D Flip-flop (edge-triggered)**  
*(positive edge triggering)*





# Delay to make sure all is well

- **Setup time**,  $t_{su}$ , is the time period prior to the clock becoming active (edge or level) during which the flip-flop inputs must remain stable.
- **Hold time**,  $t_h$ , is the time after the clock becomes inactive during which the flip-flop inputs must remain stable.
- Setup time and hold time define a *window of time during which the flip-flop inputs cannot change* – quiescent interval.


# More Delay

- **Propagation delay**,  $t_{pHL}$  and  $t_{pLH}$ , has the same meaning as in combinational circuit – beware propagation delays usually will not be equal for all input to output pairs. There can be two propagation delays:  $t_{C-Q}$  (*clock*→Q delay) and  $t_{D-Q}$  (*data*→Q delay).
- For a level or pulse triggered latch:
  - Data input should remain stable till the clock becomes inactive.
  - Clock should remain active till the input change is propagated to Q output. That is, active period of the clock,


$$t_w > \max \{t_{pLH}, t_{pHL}\}$$



# The Triggering Dilemma

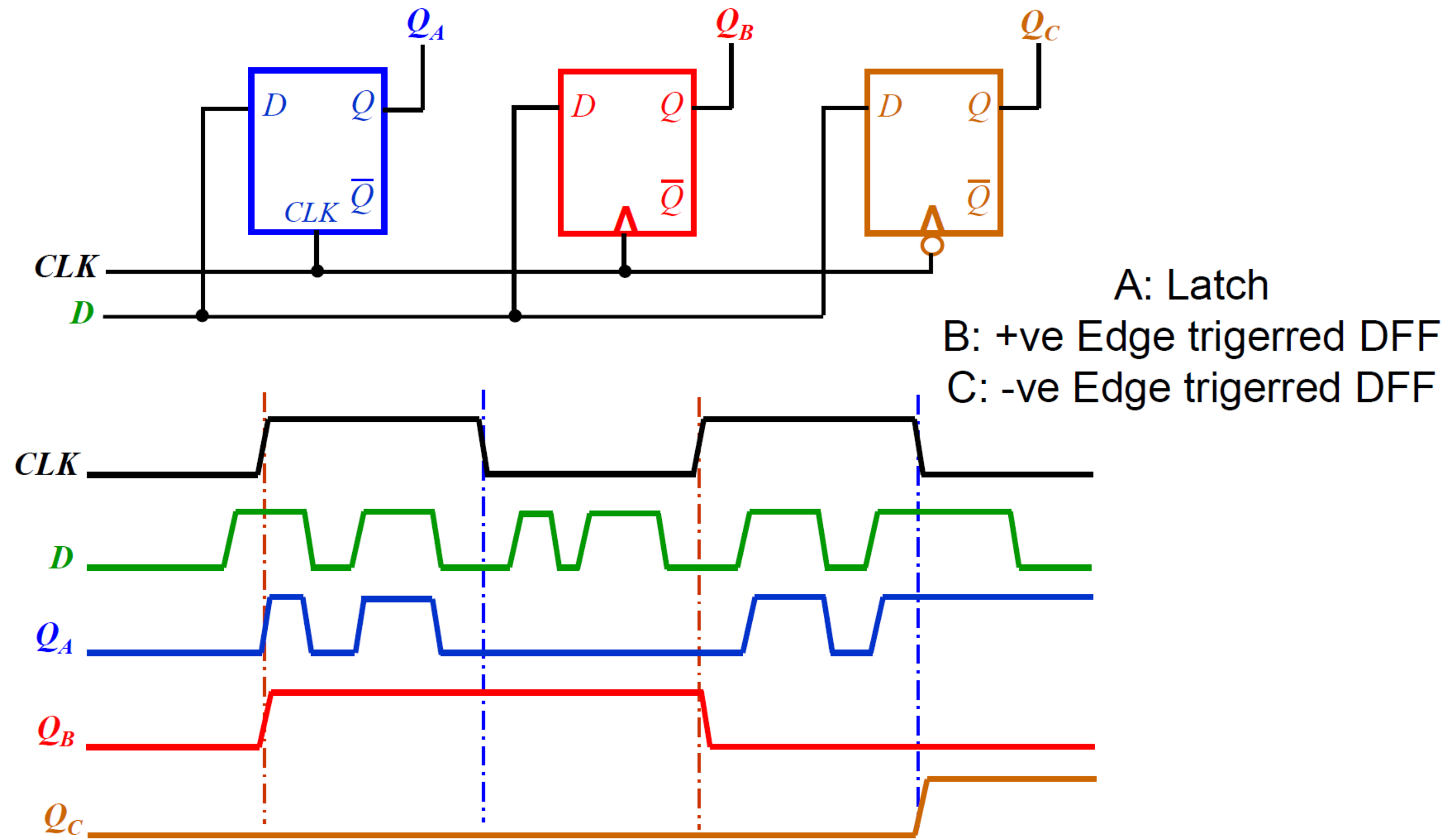

# Master Slave Flip-Flop

 

Negative edge triggered flipflop


At a given time, only one latch is alive (either master or slave)




# Master Slave Flip-Flop

**Master-slave flip-flop:** a type of synchronous memory element that eliminates the timing problems by isolating its inputs from its outputs

**Master-slave *SR* flip-flop:**

 

 **Master-slave *JK* flip-flop:** since master-slave *SR* flip-flop suffers from the problem that both its inputs cannot be 1, it can be converted to a *JK* flip-flop




# Edge Triggered Flip-Flop

**Positive (negative) edge-triggered  $D$  flip-flop:** stores the value at the  $D$  input when the clock makes a 0  $\rightarrow$  1 (1  $\rightarrow$  0) transition

- Any change at the  $D$  input after the clock has made a transition does not have any effect on the value stored in the flip-flop


 
**A negative edge-triggered  $D$  flip-flop:**

- When the clock is high, the output of the bottommost (topmost) NOR gate is at  $D'$  ( $D$ ), whereas the  $S$ - $R$  inputs of the output latch are at 0, causing it to hold previous value
- When the clock goes low, the value from the bottommost (topmost) NOR gate gets transferred as  $D$  ( $D'$ ) to the  $S$  ( $R$ ) input of the output latch
  - Thus, output latch stores the value of  $D$
- If there is a change in the value of the  $D$  input after the clock has made its transition, the bottommost NOR gate attains value 0
  - However, this cannot change the  $SR$  inputs of the output latch




 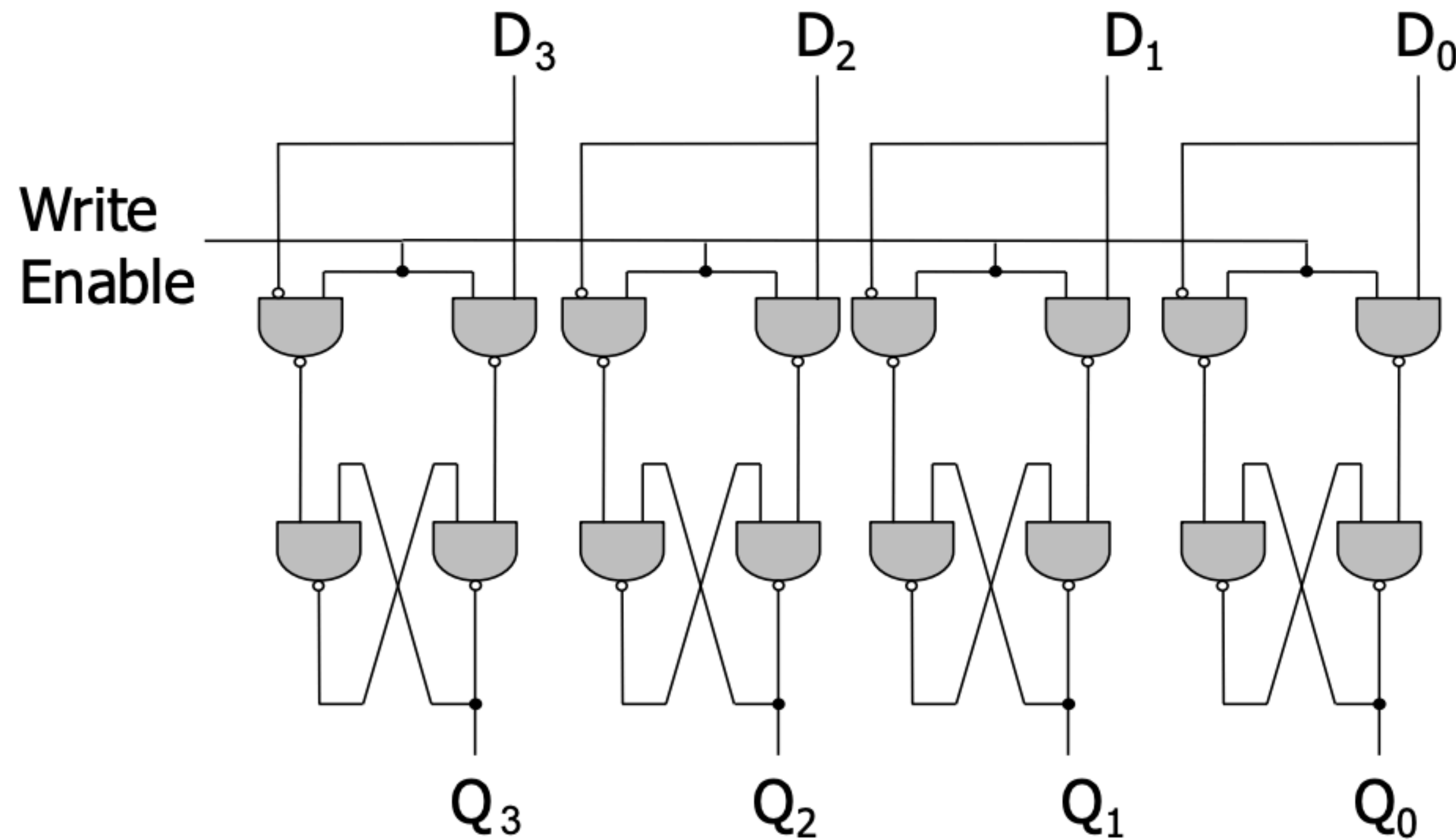
# Registers: Your Main Sequential Element



- Used to store data
- Basically an **array of D-flip-flops**
- You can **load data**, reset it to zero, and **shift it to left and right**